

Description


This Dice uses a binary display system (red LEDs) and a linear feedback regression system to simulate randomness. This is done through the use of 3 D flip flops and an XNOR. Additionally, the circuit uses a binary decoder created through NANDs, NORs and NOT gates to filter out unwanted output values (0, 7) which would not normally be seen on a regular 6-sided die.

NOTE - This system was originally intended to have a seven-segment display and decoder to display decimal values rather than binary.





Necessary Components:

Name	Quantity	Function
IC 7486	1	Quad 2-input XOR gate used for 3-bit LFSR
IC 74175	1	4-channel D FlipFlop
IC 7402	1	4-channel NOR Gates
IC 7400	1	4-channel NAND Gates
IC 7404	1	8-channel NOT Gates
7-segment Display	1	7-segment display
IC 7447	1	7-segment display decoder


Main Mapping

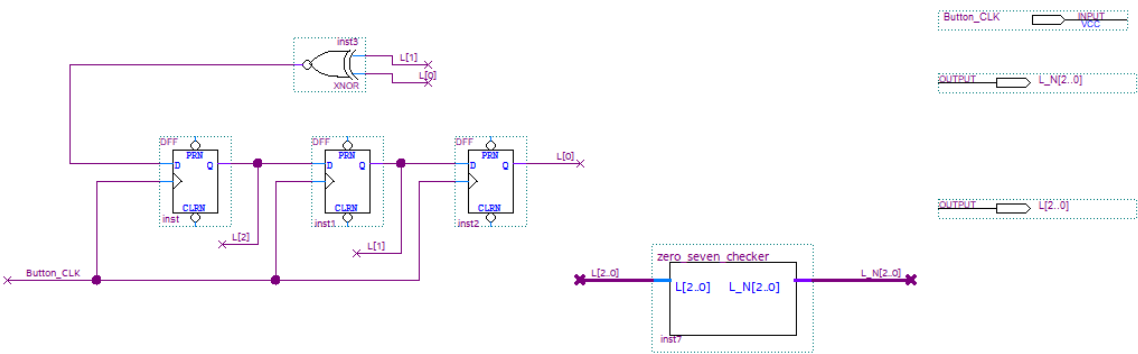

0/7 Checker

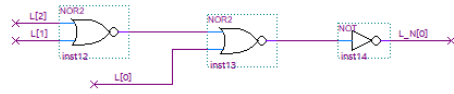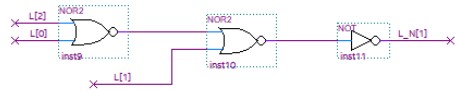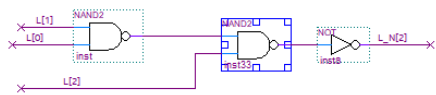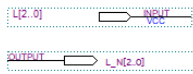

Quartus Simulation

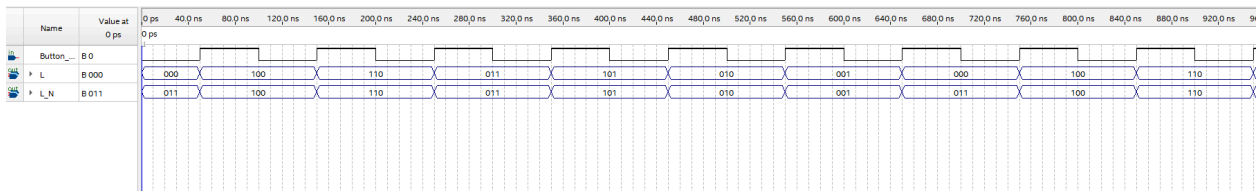

Voltage Divider

